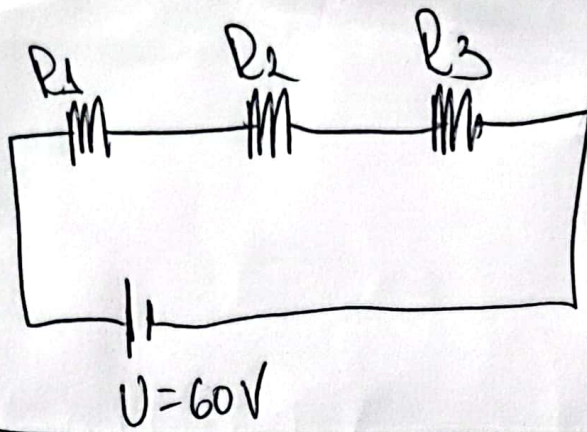


1) a)



b) $R_{eq} = R_1 + R_2 + R_3$

$R_{eq} = 5 + 10 + 15$

$R_{eq} = 30 \Omega$

c) $U = R \cdot i$

$60 = 30 \cdot i$

$i = \frac{60}{30}$

$i = 2A$

d) R_1

$U = R \cdot i$

$U = 5 \cdot 2$

$U = 10V$

R_2

$U = 10 \cdot 2$


$U = 20V$

R_3

$U = 15 \cdot 2$

$U = 30V$

2) a)

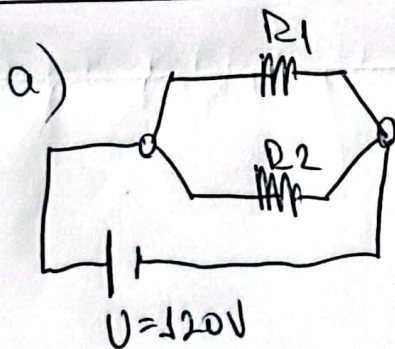


b) $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

$\frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{30}$

$\frac{1}{R_{eq}} = \frac{3 + 2}{60}$

$R_{eq} = \frac{60}{5} = 12 \Omega$

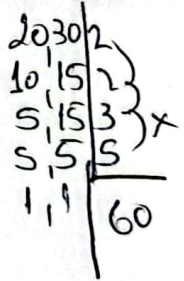

c) $U = R \cdot i$

$120 = 12 \cdot i$

$i = \frac{120}{12}$

$i = 10A$

d)

R_1

$U = R \cdot i$

$120 = 20 \cdot i$

$i = \frac{120}{20}$

$i = 6A$

R_2

$U = R \cdot i$

$120 = 30 \cdot i$

$i = \frac{120}{30}$

$i = 4A$